

**Aim** ⇨ To study the input and output characteristics of a Bipolar Junction Transistor connected in a Common Base configuration.

**Equipment Required** ⇨

Bipolar Junction Transistor, Resistance, Power supply, Ammeter, Voltmeter, Breadboard and connecting wires.

**Theory** ⇨

A Bipolar Junction Transistor (BJT) is a three-terminal semiconductor device used for amplification and switching, comprising three regions: the emitter, the base, and the collector. BJTs come in two types, NPN and PNP, with the primary difference being the polarity of the voltages and the direction of the currents. In a common base (CB) configuration, the base terminal is common to both the input and the output circuits. The input signal is applied between the emitter and the base, and the output is taken from the collector and the base.

The input characteristics of a BJT in CB configuration describe the relationship between the emitter current ( $I_E$ ) and the base-emitter voltage ( $V_{BE}$ ) for various levels of collector-base voltage ( $V_{CB}$ ). These characteristics are observed by varying  $V_{BE}$  and measuring  $I_E$  while keeping  $V_{CB}$  constant. In the forward active region, the emitter-base junction is forward-biased, resulting in a large change in  $I_E$  for a small change in  $V_{BE}$ .

The output characteristics describe the relationship between the collector current ( $I_C$ ) and the collector-base voltage ( $V_{CB}$ ) for different levels of emitter current ( $I_E$ ). These are obtained by varying  $V_{CB}$  and measuring  $I_C$  while keeping  $I_E$  constant. In the active region, the emitter-base junction is forward-biased and the collector-base junction is reverse-biased, resulting in  $I_C$  being largely independent of  $V_{CB}$  and primarily determined by  $I_E$ . The saturation region occurs when  $V_{CB}$  is low, and both junctions are forward-biased, leading to improper amplification. The cutoff region is when both junctions are reverse-biased, and the transistor is in the off state with minimal current flow.

The common base configuration is characterized by high voltage gain, low input impedance, and high output impedance. The input impedance is low because the input is applied to the forward-biased emitter-base junction, while the output impedance is high due to the reverse-biased collector-base junction. The current gain ( $\alpha$ ), which is the ratio of the collector current to the emitter current ( $\alpha = \frac{I_C}{I_E}$ ), is typically less than 1 but very close to 1.

The common base configuration is used in applications requiring high-frequency operation, impedance matching, and voltage gain without current gain. The primary objectives of studying the input and output characteristics of a BJT in this configuration are to plot the input characteristic curves ( $I_E$  vs.  $V_{BE}$  for different values of  $V_{CB}$ ) and the output characteristic curves ( $I_C$  vs.  $V_{CB}$  for different values of  $I_E$ ). Understanding these characteristics is essential for designing and analyzing circuits using BJTs in the common base configuration.

### Circuit Diagram ↗

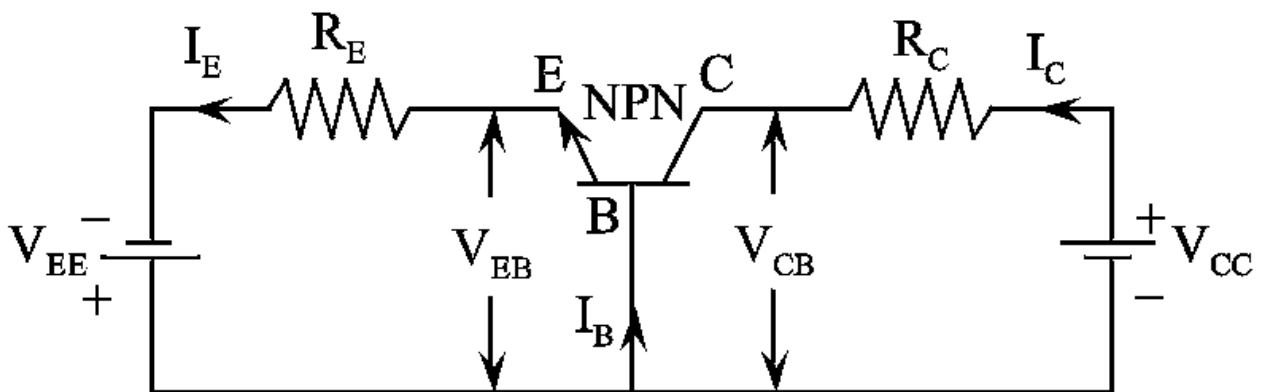


Fig 1. npn transistor in common base configuration

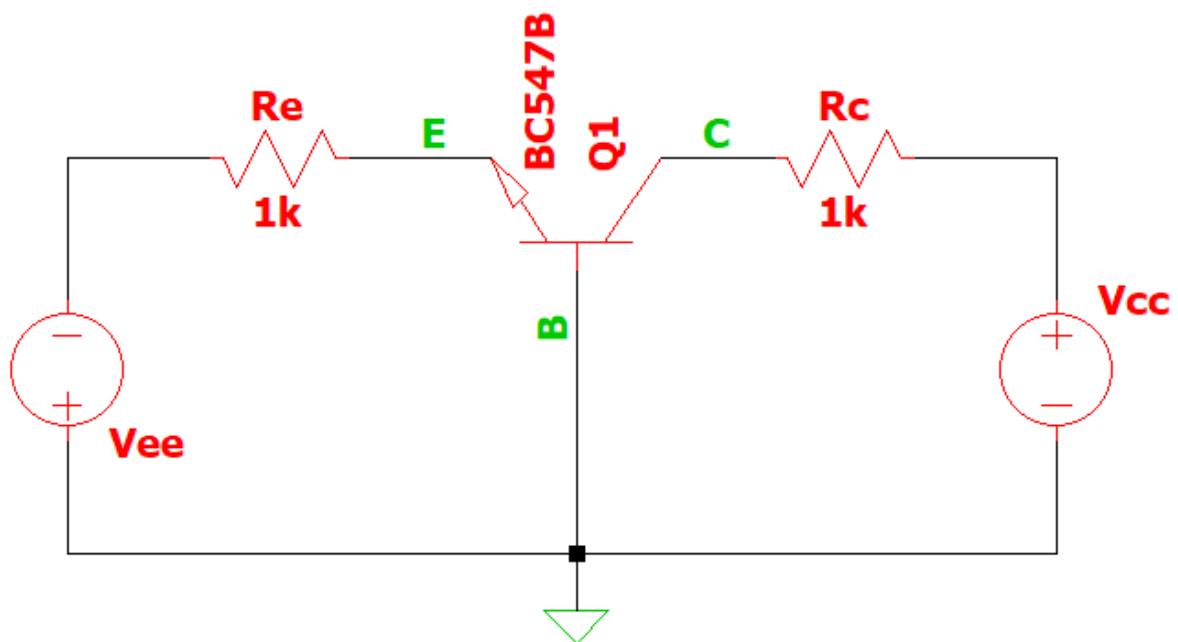


Fig 2. Circuit in LTSpice

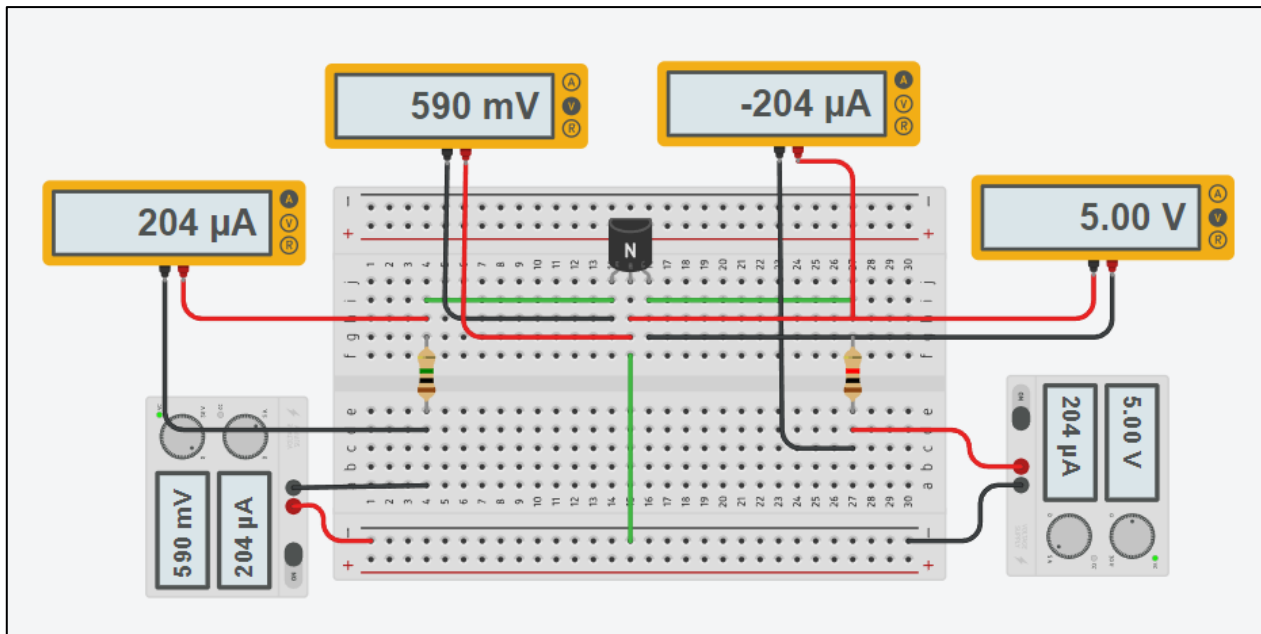


Fig 4. Circuit in Tinkercad

## Observation Table ↷

### ➤ Input Characteristics ↷

S.No.	V <sub>ee</sub> (V)	V <sub>cc</sub> = 0V		V <sub>cc</sub> = 5V		V <sub>cc</sub> = 10V	
		I <sub>e</sub> (μA)	V <sub>be</sub> (V)	I <sub>e</sub> (μA)	V <sub>be</sub> (V)	I <sub>e</sub> (μA)	V <sub>be</sub> (V)
1	0.1	0	0.1	0	0.1	0	0.1
2	0.2	0	0.2	0	0.2	0	0.2
3	0.3	0	0.29	0	0.29	0	0.29
4	0.4	0.11	0.39	0.12	0.39	0.13	0.39
5	0.5	4.26	0.49	4.55	0.49	4.83	0.49
6	0.6	43.55	0.55	44.81	0.55	46	0.55
7	0.8	203	0.59	205	0.59	207	0.59
8	1.0	386	0.61	388	0.61	390	0.61
9	1.5	842	0.66	866	0.63	868	0.63
10	2.0	1315	0.68	1354	0.65	1356	0.64

➤ Output Characteristics ↔

S.No.	Vcc(V)	Vee = 2V		Vee = 5V		Vee = 10V	
		Ic(mA)	Vcb(V)	Ic(mA)	Vcb(V)	Ic(mA)	Vcb(V)
1	0	0.75	-0.75	0.81	-0.805	0.83	-0.831
2	0.1	0.85	-0.74	0.91	-0.804	0.93	-0.829
3	0.2	1.03	-0.73	1.10	-0.803	1.13	-0.828
4	0.5	1.18	-0.68	1.30	-0.801	1.33	-0.827
5	0.8	1.22	-0.42	1.59	-0.798	1.62	-0.826
6	1	1.22	-0.22	1.79	-0.796	1.83	-0.825
7	2	1.22	0.78	2.78	-0.782	2.82	-0.822
8	5	1.22	3.78	4.17	0.825	5.80	-0.805
9	8	1.22	6.78	4.17	3.825	8.75	-0.750
10	10	1.22	8.78	4.17	5.825	9.14	0.862

Graphs ↔

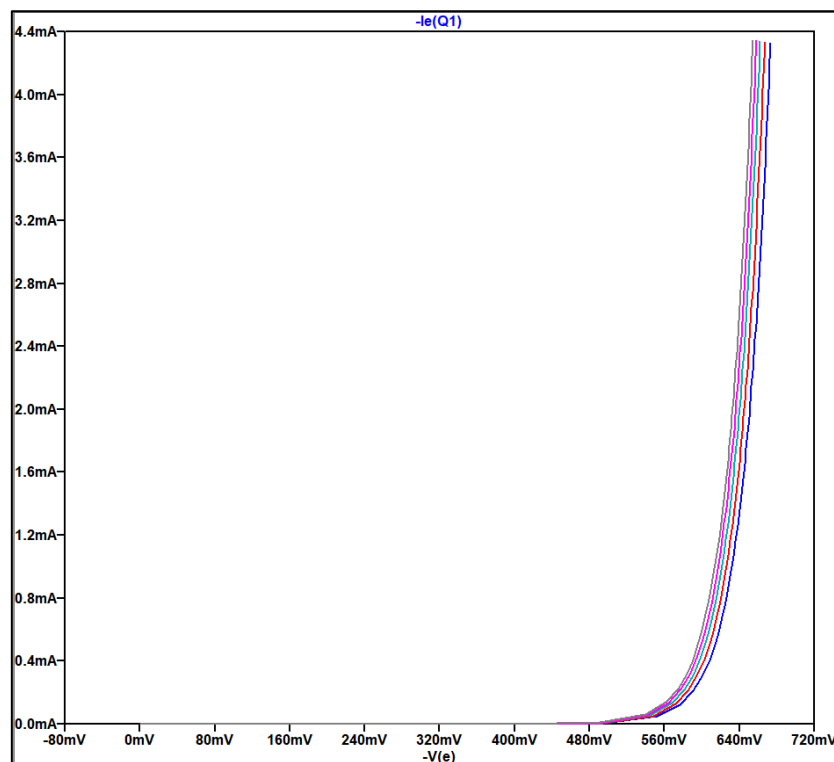


Fig 6. Input Characteristics

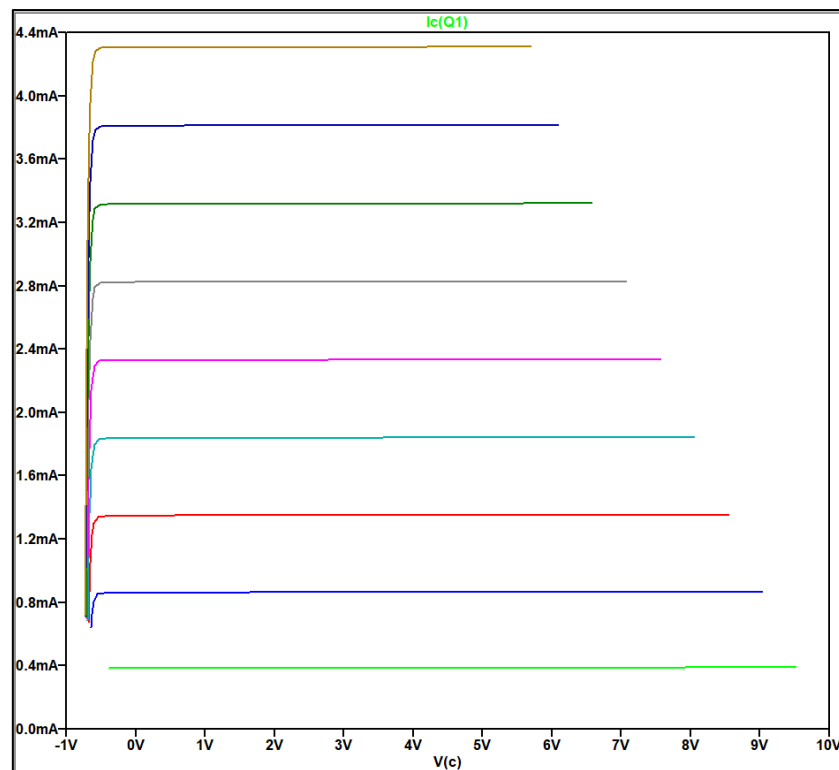


Fig 7. Output Characteristics

## Result ⇄

The experiment revealed that in a common base configuration, the emitter current  $I_E$  increased significantly with base-emitter voltage  $V_{BE}$  while keeping the collector-base voltage  $V_{CB}$  constant. The collector current  $I_C$  remained relatively stable across various  $V_{CB}$  levels for fixed  $I_E$ , indicating  $I_C$  is controlled mainly by  $I_E$ . These results confirm the expected behaviour of high voltage gain, low input impedance, and high output impedance, validating the theoretical predictions for the common base configuration of a BJT.

## Conclusion ⇄

Successfully performed the experiment and matched the result with the simulation result.

## Precautions ⇄

- While doing the experiment, do not exceed the ratings of the transistor. This may lead to damage to the transistor.
- Connect the Voltmeter and Ammeter in the correct polarities as shown in the circuit diagram.
- Do not switch ON the power supply unless you have checked the circuit connections as per the circuit diagram.