

Aim ⇨ To design and obtain the frequency response of First Order Low Pass Filter [LPF].

Equipment Required ⇨

Resistance, Potentiometer, Capacitor, IC 741 OP-AMP, Function Generator, CRO, Breadboard & connecting wires.

Theory ⇨

A low-pass filter allows signals with frequencies lower than a specified cut-off frequency f_H to pass through while attenuating frequencies higher than f_H . At the cut-off frequency, the gain of the LPF is reduced to 70.7% (or -3 dB) of its maximum value. This point, where the filter transitions from passing to attenuating frequencies, is crucial for defining the filter's performance.

Roll-off Rate and Filter Order ↴

A First Order LPF exhibits a roll-off rate of 20 dB/decade or 6 dB/octave. This means that for every tenfold increase in frequency, the gain drops by 20 dB, or for every doubling of frequency, it drops by 6 dB.

Higher-order filters exhibit steeper roll-off rates, making first-order filters suitable for applications where a gradual attenuation of higher frequencies is acceptable.

Mathematical Expression ↴

$$f_H = \frac{1}{2\pi RC}$$

This formula derives from the basic principles of filter design, where the cut-off frequency is inversely proportional to the product of resistance and capacitance.

Practical Considerations ↴

The cut-off frequency is also known as the -3 dB frequency, break frequency, or corner frequency. It is a critical parameter in determining how effectively the filter can separate desired signals from unwanted high-frequency noise.

In practical applications, LPFs are used to filter out high-frequency noise from signals, ensuring that only the relevant lower-frequency components are processed. This is essential in audio processing, signal conditioning, and many other electronic applications.

Circuit Diagram ⇄

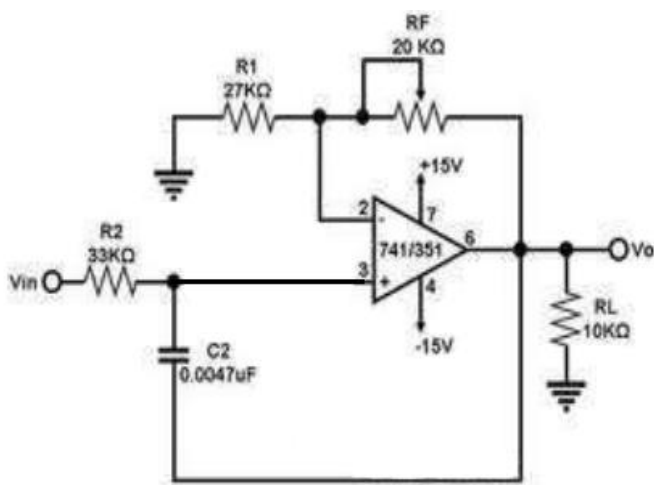


Fig. i) First Order Low Pass Filter

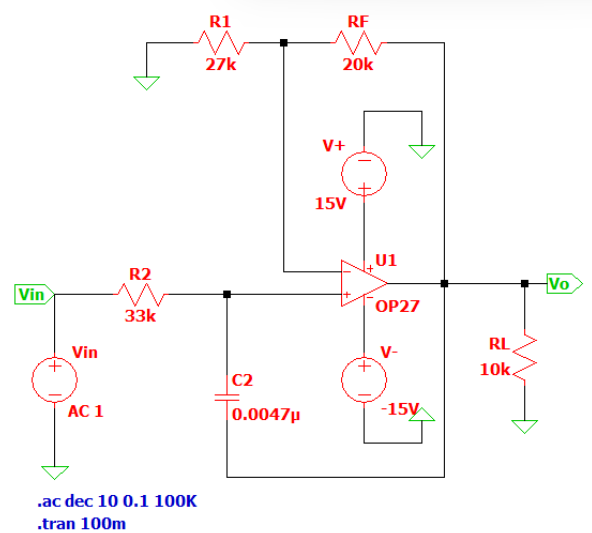


Fig. ii) LTSpice Implementation

Observation Table ⇄

▪ Simulation Data ⇄

S.No.	Input Freq f [Hz]	Gain Magnitude $\left \frac{V_o}{V_i} \right $	Magnitude in dB $20 \log \left \frac{V_o}{V_i} \right $
1	0.1	1.76	4.89
2	1	1.74	4.83
3	10	1.74	4.82
4	100	1.73	4.73
5	1K	1.42	2.98
6	10K	237m	-12.5
7	100K	24.3m	-32.3

Graphs ⇄

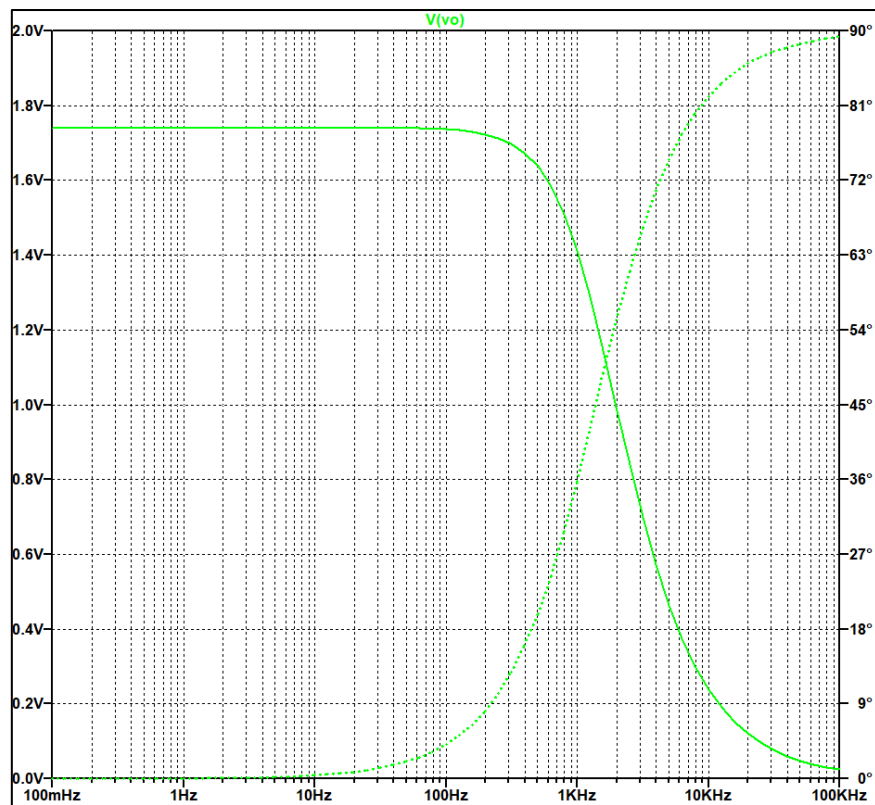


Fig. iii) Frequency Response [Linear]

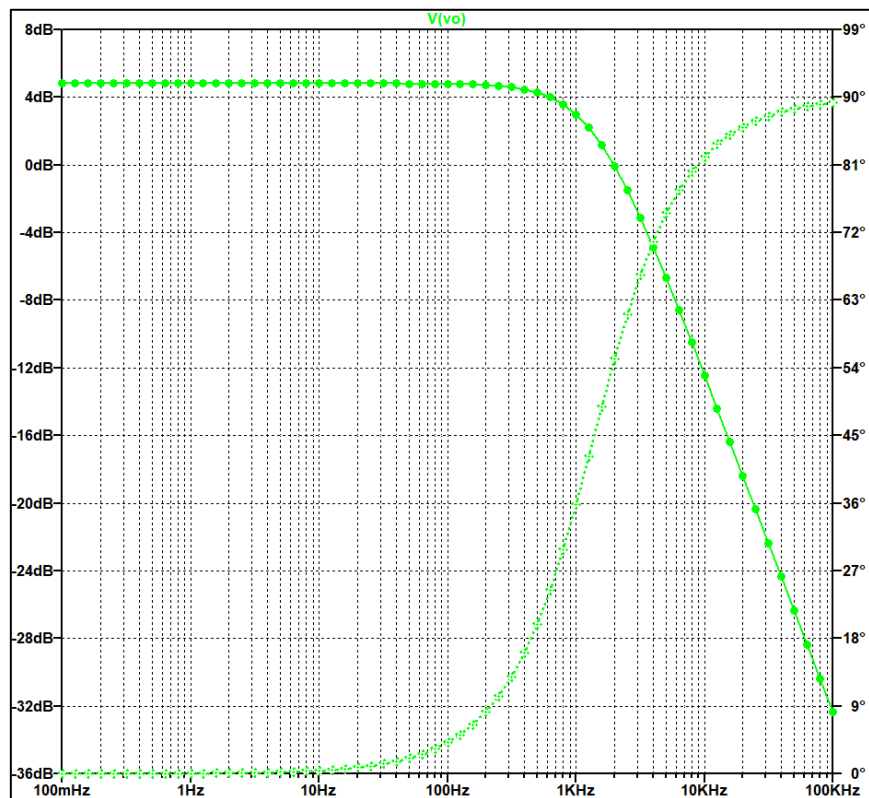


Fig. iv) Frequency Response [Decibel]

Output ⇌



Fig. v) DSO Output with increasing frequency

Result ⇌

The experiment demonstrated the design and frequency response of a first-order low-pass filter. The filter passed signals below the cut-off frequency f_H and attenuated higher frequencies at 20 dB/decade, as expected.

Conclusion ⇌

The first-order low-pass filter was designed and tested successfully, matching the expected theoretical and simulation results. The filter exhibited the correct frequency response with the predicted roll-off rate beyond the cut-off frequency.

Precautions ⇌

- Ensure all connections are correct and components are securely placed.
- Do not exceed the voltage ratings of components, especially the op-amp.
- Verify capacitor polarity and op-amp orientation.
- Double-check the circuit setup before powering on the equipment.